



Circuiti Digitali



NOT

A	Y
0	1
1	0




“Inverter logico”



Porta AND



A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 

“Prodotto logico”



Porta OR



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1




“Somma logica”



Porta NOR



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

 


“Not(Or(A,B))”



Porta NAND




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

 

“Not(And(A,B))”



Circuiti di base

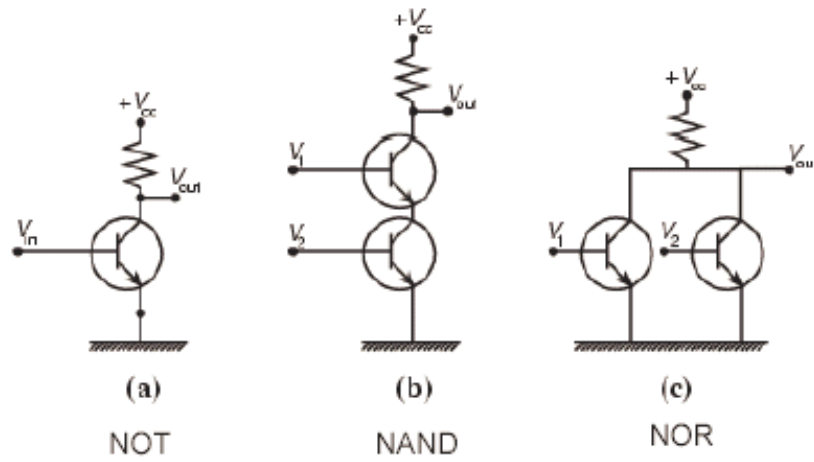


Copyright @ Alberto Borghese, 2001

<http://www.inb.mi.cnr.it/Borghese.html>



Logica RTL

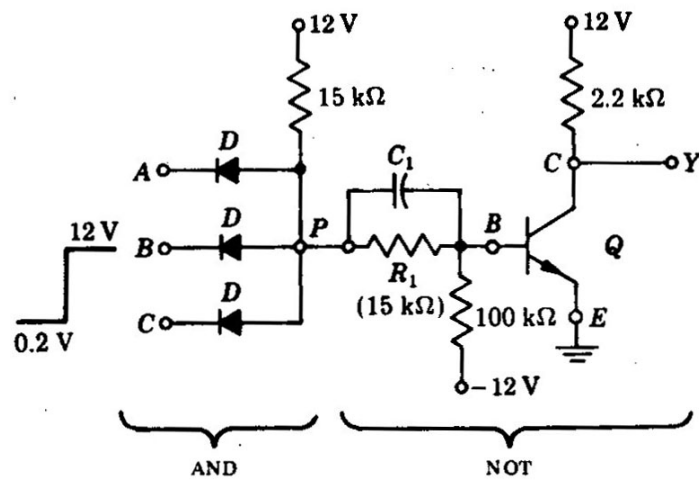


Porta NAND a 3 ingressi in Resistor Transistor Logic (RTL).

Copyright @ Alberto Borghese, 2001

<http://www.inb.mi.cnr.it/Borghese.html>



Logica TTL

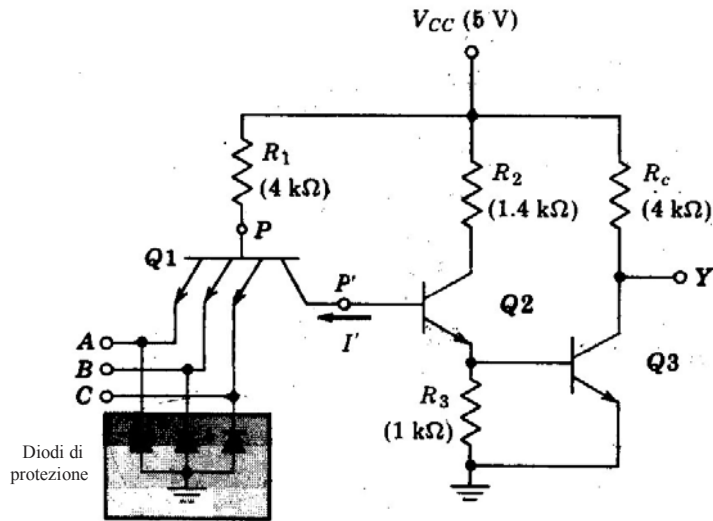

Porta NAND in Transistor-Transistor-Logic.


Copyright @ Alberto Borghese, 2001

<http://www.inb.mi.cnr.it/Borghese.html>



Logica TTL three-state

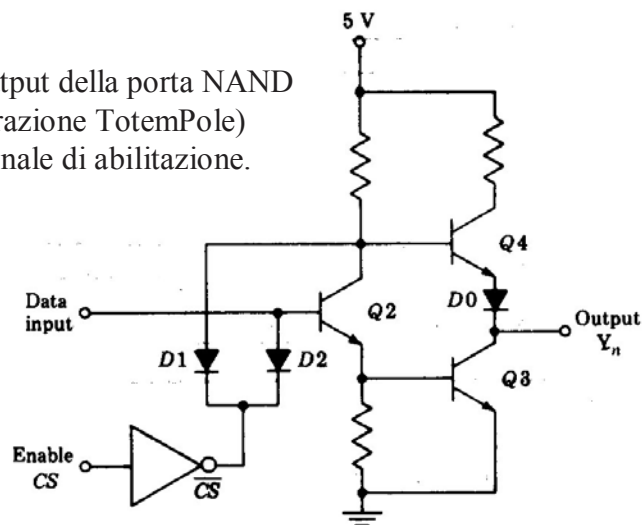Stadio di output della porta NAND
(configurazione TotemPole)
con il segnale di abilitazione.



CS = 0 → Chip enabled

Copyright @ Alberto Borghese, 2001

<http://www.inb.mi.cnr.it/Borghese.html>



Logica TTL three-state



Stadio di output della porta NAND
(configurazione TotemPole)
con il segnale di abilitazione.

